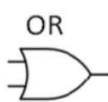



Ingangen		Uitgang
P ₁	P ₂	Q
0	0	0
0	1	0
1	0	0
1	1	1

$$\text{AND} = P_1 \cdot P_2$$




Ingangen		Uitgang
P ₁	P ₂	Q
0	0	0
0	1	1
1	0	1
1	1	1

$$\text{OR} = P_1 + P_2$$

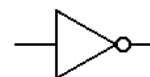


Ingang	Uitgang
P	Q
1	0
0	1

$$\text{NOT} = \overline{N}$$

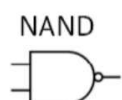

Ingangen		Uitgang
P ₁	P ₂	Q
0	0	1
0	1	1
1	0	1
1	1	0

$$\text{NAND} = P_1 \odot P_2$$

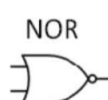

Ingangen		Uitgang
P ₁	P ₂	Q
0	0	1
0	1	0
1	0	0
1	1	0


$$\text{NOR} = \overline{P_1 + P_2}$$



Ingangen		Uitgang
P ₁	P ₂	Q
0	0	0
0	1	1
1	0	1
1	1	0

$$\text{XOR} = A \oplus B$$

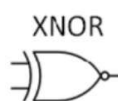Q is 1 als er **een verschil** tussen de ingangen is



Ingangen		Uitgang
P ₁	P ₂	Q
0	0	1
0	1	0
1	0	0
1	1	1

$$\text{XNOR} = \overline{P_1 \oplus P_2}$$

Q is 1 als er **geen verschil** is tussen de ingangen